

ELECTRONIC CIRCUITS AND COMMUNICATION FUNDAMENTALS

- Explain the construction of n-channel JFET
- List the ideal Characteristics of Op-amp
- What is modulation in communication? What is the need for modulation?
- Compare TDM and FDM
- Explain Barkhausen Criteria for Oscillation. Calculate the frequency of oscillations of Colpitt's oscillator with $C_1 = C_2 = 500 \text{ pF}$ and $L = 1 \text{ mH}$
- Derive the equations for Z_i, Z_o, A_v for common source configuration using voltage divider network
- Explain how op-amp can be used as averaging amplifier in inverting configuration
- Explain generation of SSB using phase shift method.
- Explain Superheterodyne receiver in detail and show waveforms at each stage
- State and proof Sampling theorem for Low pass Signal.
- Discuss Delta Modulation and Adaptive Delta Modulation
- Write short note on TDM-PCM System
- Write Short note on a) PLL b) Op-amp as Comparator